


Name: Anshuman Mondal
 Roll No: - 230102009
 Branch: ECE

EE-206

OTA Assignment


Circuit Diagram: (2 Stage OTA analysis - AC)

$V_{DD} = 1.2V$

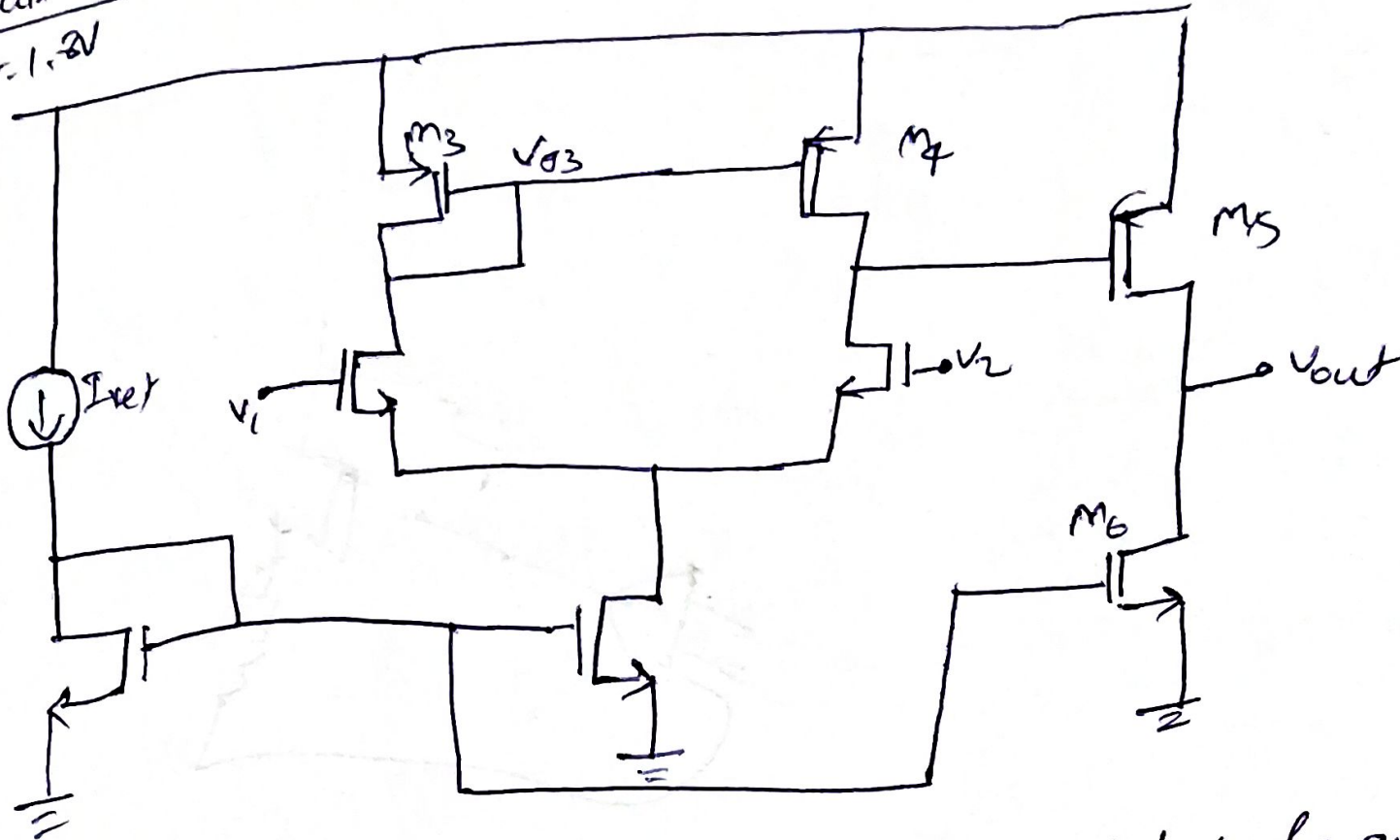


* Calculations: $V_2 \rightarrow$ is the AC signal of $50\mu V$ amplitude for $0.9V_{DC}$ (offset)
 $V_1 = 0.9V_{DC}$, $50\mu V$ opposite phase (180° out of phase) { for maximum swing, the output doesn't clip }

* Closed loop:

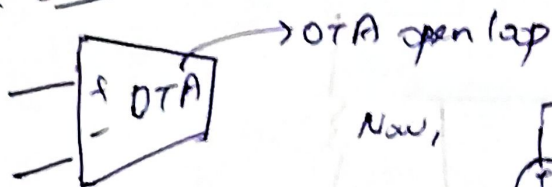

Now,

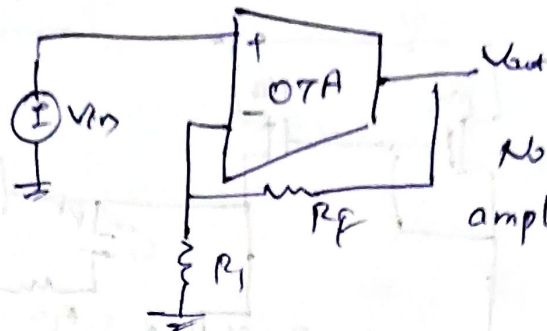


Now considering infinite amplification,
 $V_+ = V_- = V_{in}$

So, applying KCL at V_-

$$\text{we get, } \frac{V_- - V_{out}}{R_F} + \frac{V_-}{R_I} = 0 \Rightarrow \frac{V_{out}}{V_-} = \frac{R_I R_F}{R_I} = \boxed{1 + \frac{R_F}{R_I}}$$

So, if $R_F = R_I$ we get 2 & $\boxed{R_F = R_I = 10.2 \text{ k}\Omega}$

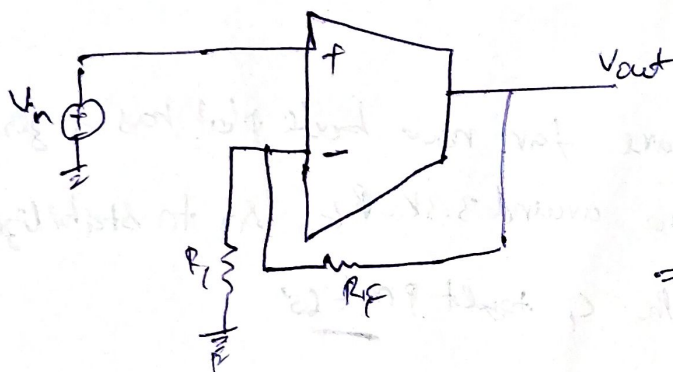but the OTA, we have designed has a finite A
 i.e., 4862.95



$$\begin{aligned} V_+ &= V_{in} \\ V_{out} &= (V_+ - V_-)A \\ \Rightarrow V_{out} - A V_{in} &= -A V_- \\ \Rightarrow \boxed{V_-} &= \frac{A V_{in} - V_{out}}{A} \end{aligned}$$

So, using KCL at V_-

$$\left(\frac{A V_{in} - V_{out}}{A} \right) \frac{1}{R_I} + \left(\frac{A V_{in} - V_{out}}{A} - V_{out} \right) \frac{1}{R_F} = 0 \Rightarrow \frac{V_{in}}{R_I} + \frac{V_{in}}{R_F} = V_{out} \left[\frac{1}{A R_I} + \frac{1}{R_F} + \frac{1}{A R_F} \right]$$

$$V_{in} \left(\frac{R_I + R_F}{R_I R_F} \right) = V_{out} \left[\frac{R_F + A R_I + R_I}{A R_I R_F} \right]$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{A(R_I + R_F)}{A R_I + R_I + R_F} = \left(1 + \frac{R_F}{R_I} \right) \left(\frac{A}{(A+1) + \frac{R_F}{R_I}} \right)$$




for closed loop system, $G_{\text{closed}} = \frac{G}{1 + GH} = \frac{4862.95}{1 + 4862.95(0.5)}$

$$\boxed{H = \left(1 + \frac{R_F}{R_I} \right)^{-1}} = 0.5$$

$$= \boxed{1.99}$$

Closed loop circuit Diagram:

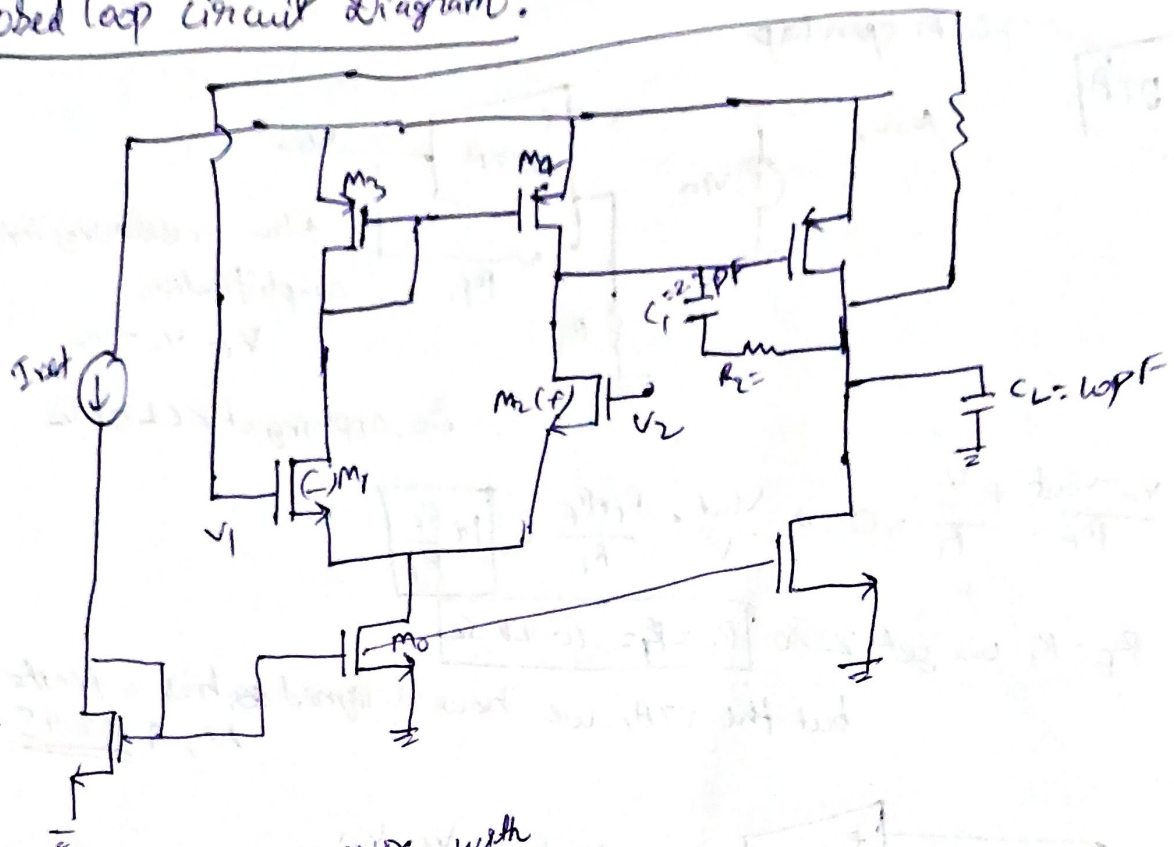

$V_1 = 0.9\text{V DC}$, $V_2 = 0.9\text{V DC}$ with

Taken, $C_1 = 2.2\text{pF}$, $C_L = 10\text{pF}$, poles are far now bode plot has a zero due to which I got a $\text{PM} \approx 70^\circ$ around $3.3\text{k} = R_2$ so to stabilize it I adjusted R_2 in series with C_1 to get $\text{PM} = 60^\circ$

I chose $R_2 = 3.3\text{k}\Omega$ for which I have my phase margin $\approx 60^\circ$ (observed)

Bandwidth observed (f_{3dB}) $\approx 9.99\text{MHz}$

* Location of dominant poles of the system:

$$\omega_p = \frac{1}{A_1 (\sqrt{g_1} \times 10^6)} = \frac{10^{12} \times 10^6}{33.864 \times 2.2 \times 0.33}$$

$$= 10^6 \times 0.0406$$

$$= 40.6\text{kHz}$$

$$A_2 (\text{practical}) = \frac{486298}{1936} = 33.864$$

$$r_{q5} = r_{q2} \approx 0.667\text{M}\Omega$$

~~Closed loop~~

Closed Loop:

Theoretical gain of overall circuit ≈ 1.99

Practical gain

Gain
needed = 2

Observed from simulation = $\frac{19.65 \text{ mV}}{10 \text{ mV}}$


$\frac{V_{out(PP)}}{V_{in(PP)}}$

$\approx \boxed{1.965}$


\therefore error = -1.256%


for 0.2 V step input, $V_{observed} = (898 - 1299.42) = 396 \text{ mV}$, $\text{Gain} = 1.98$
'pc' analysis was attached in pc simulation file, previously uploaded

doing doing

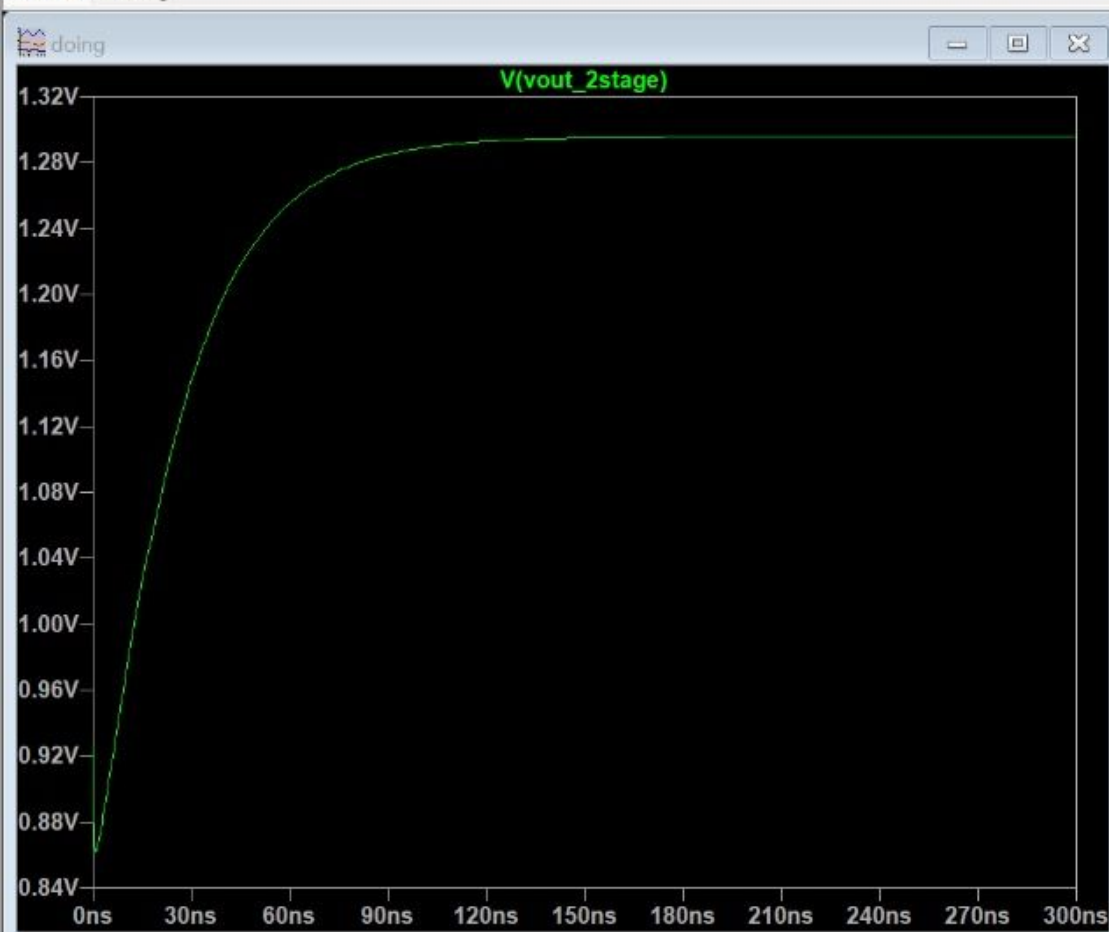


x = 15.71ns y = 1.3378V

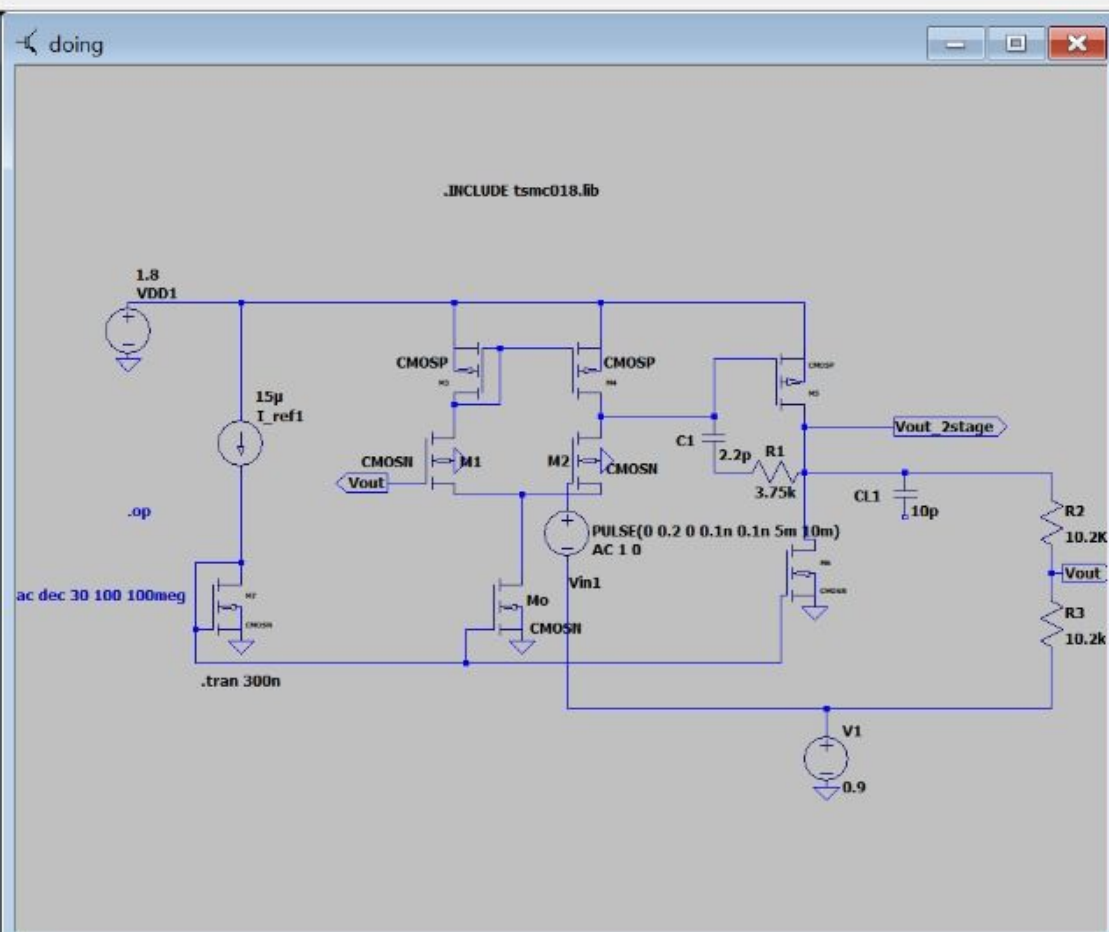


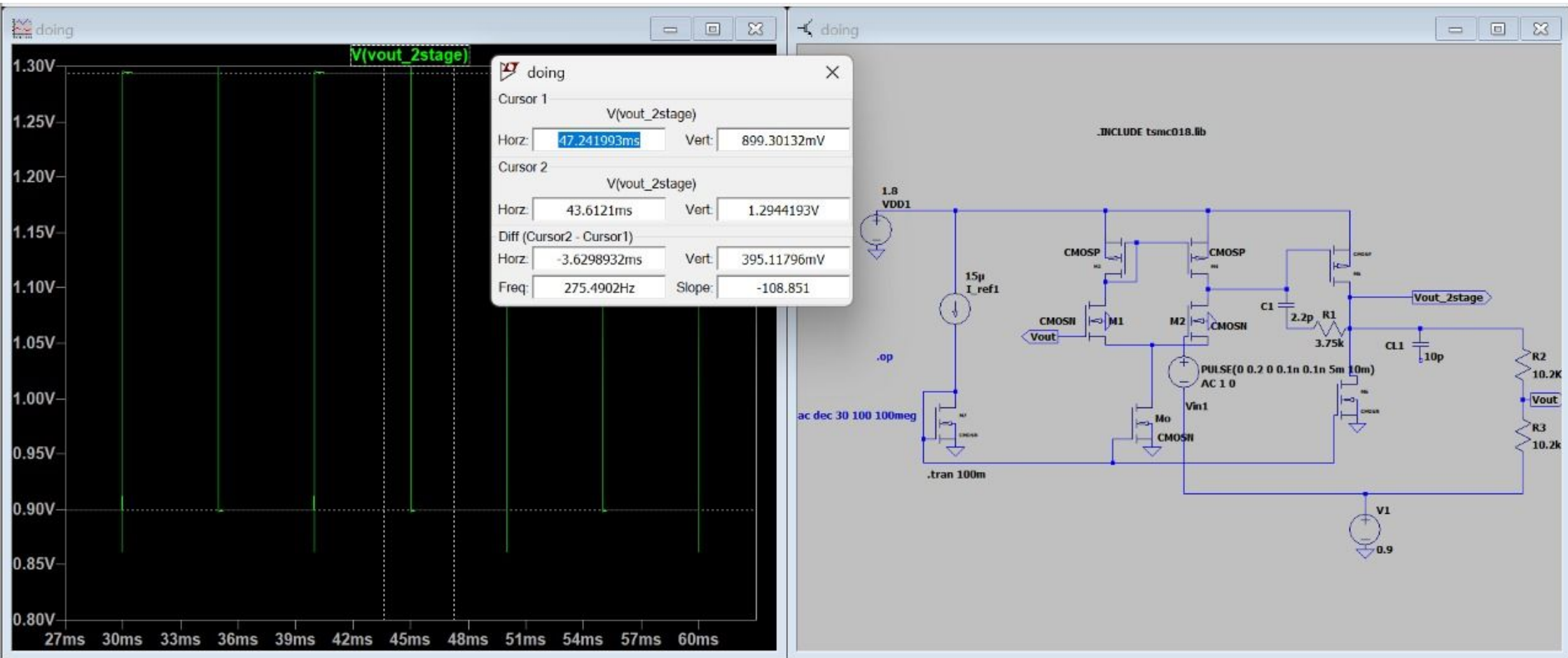


Left-Click & drag to move Cursor 1

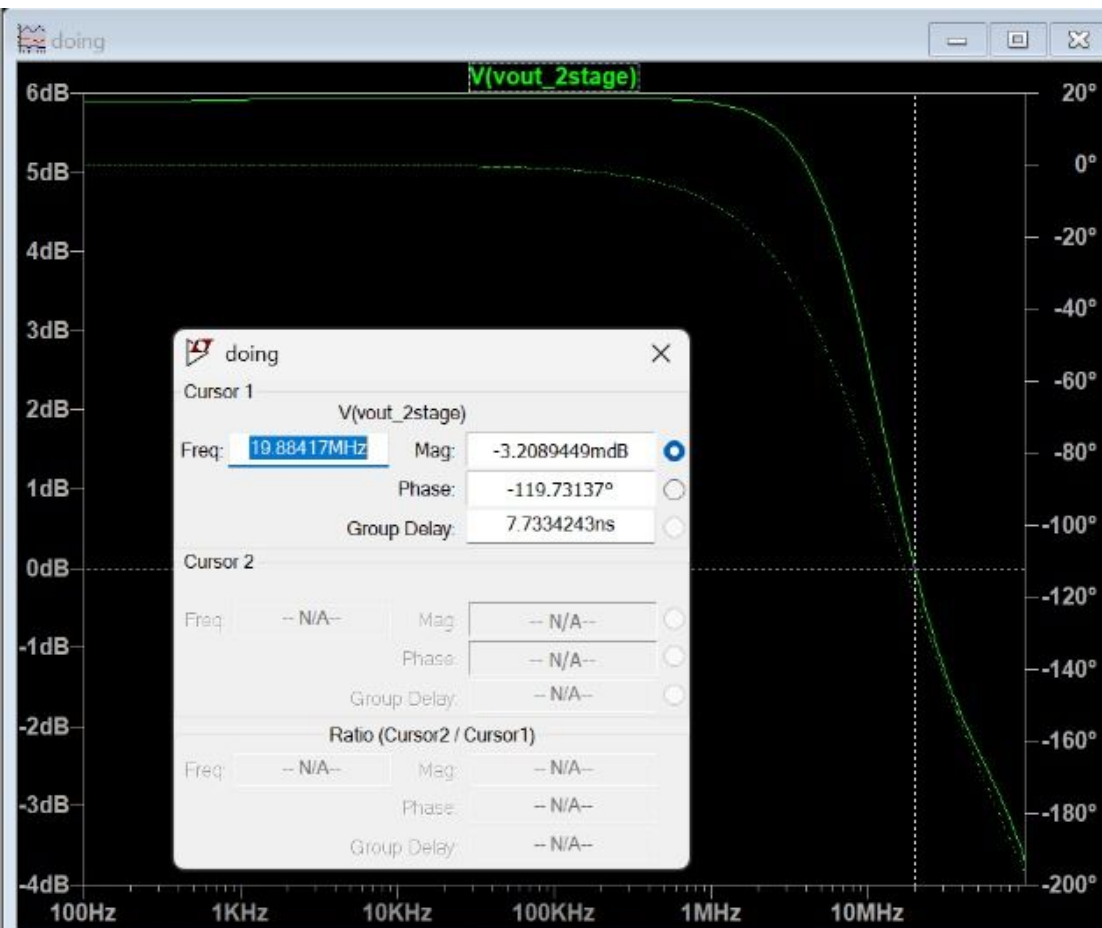


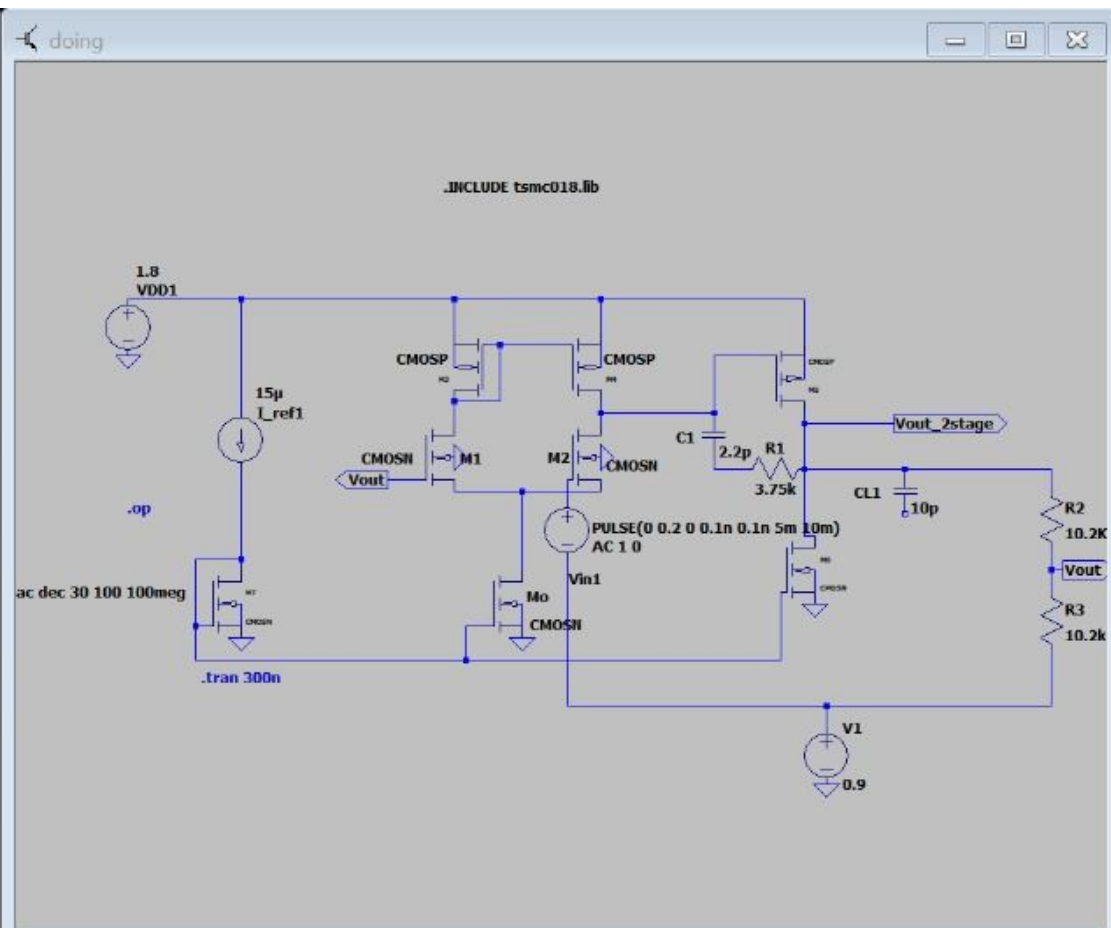
$x = 5.672\text{KHz}$ $y = 4.077\text{dB}, -22.308^\circ$




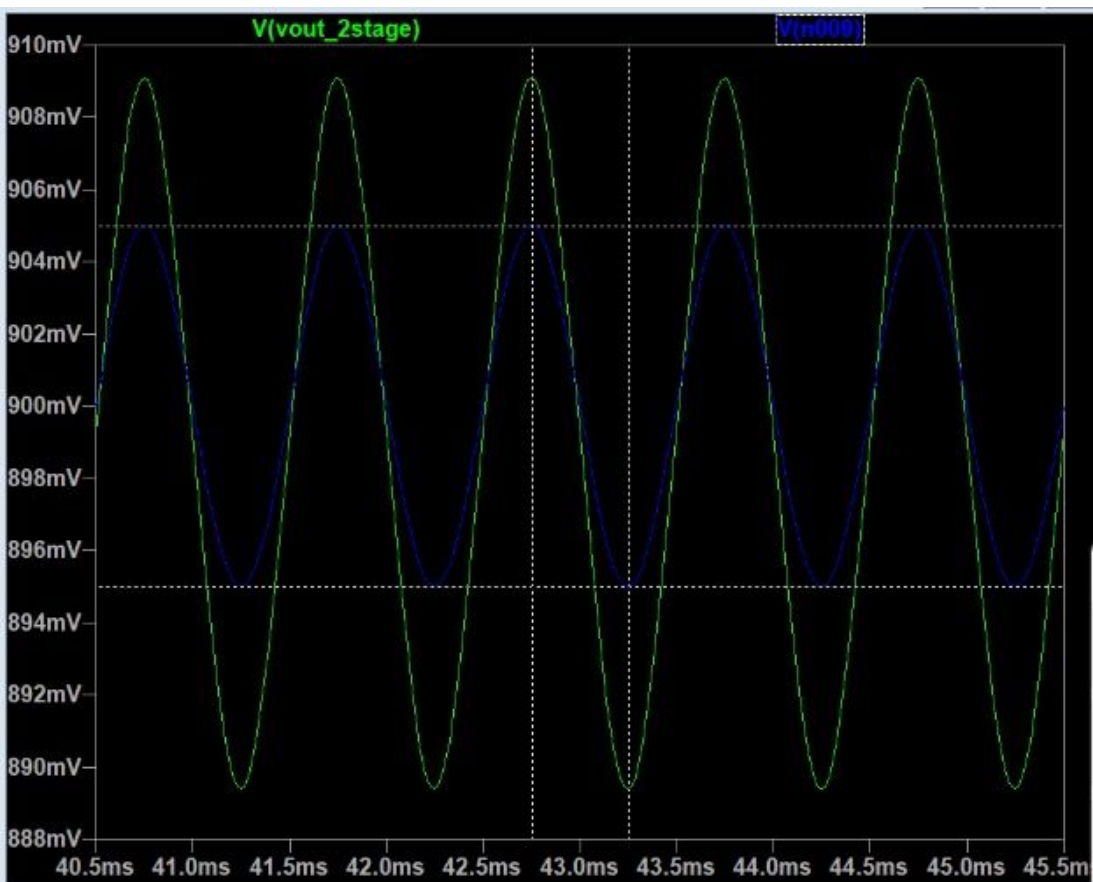


x = 40.761ms y = 909.09mV

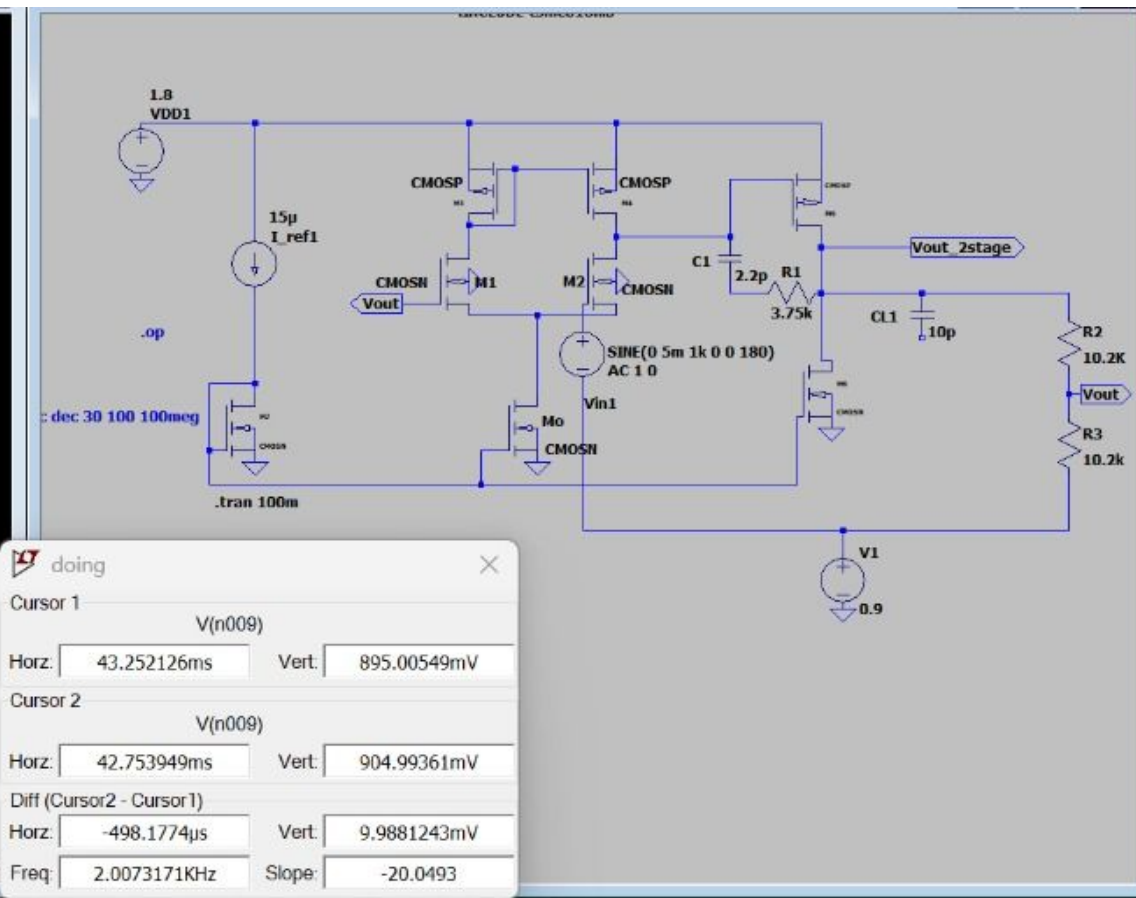

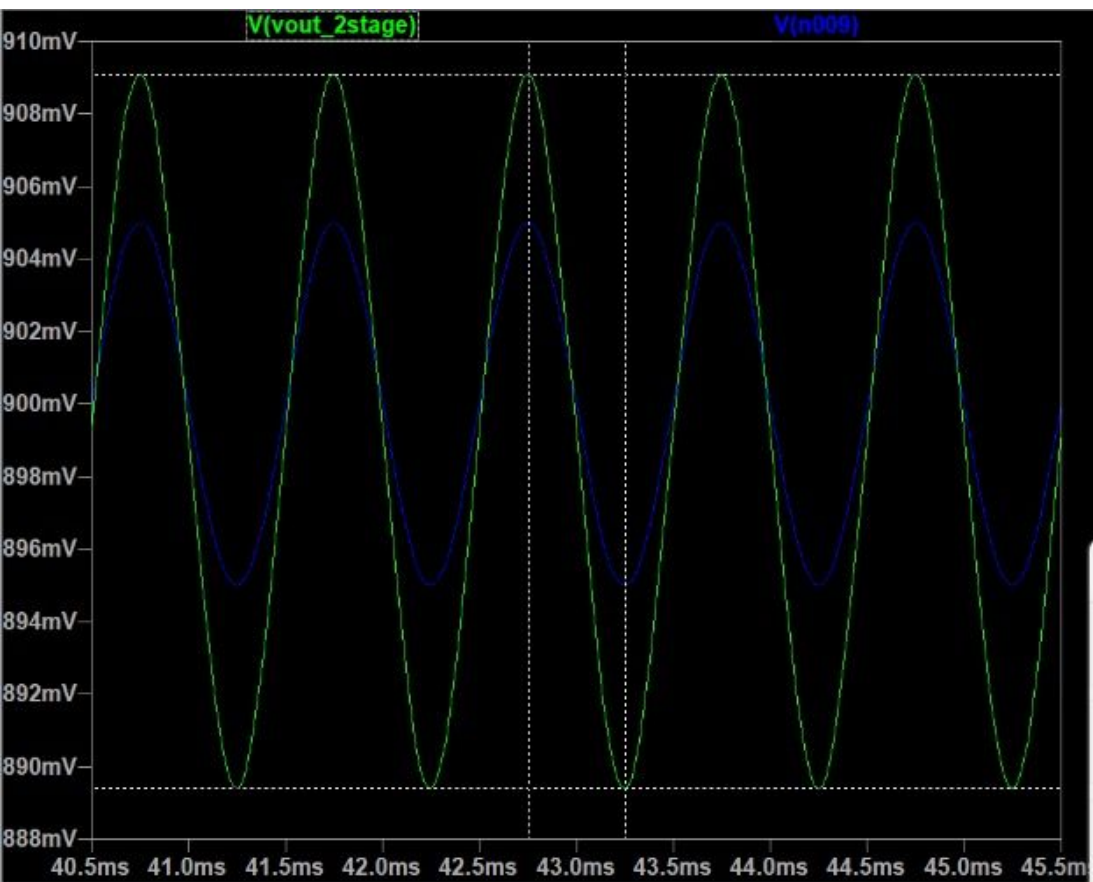

x = 40.524ms y = 910.81mV

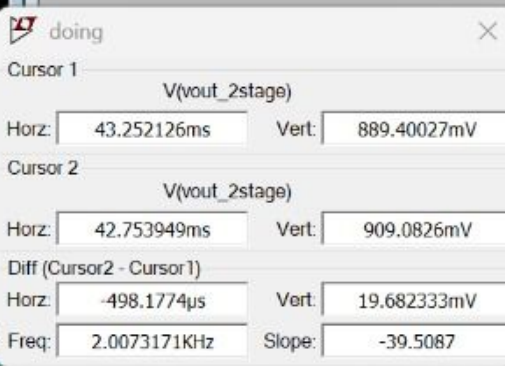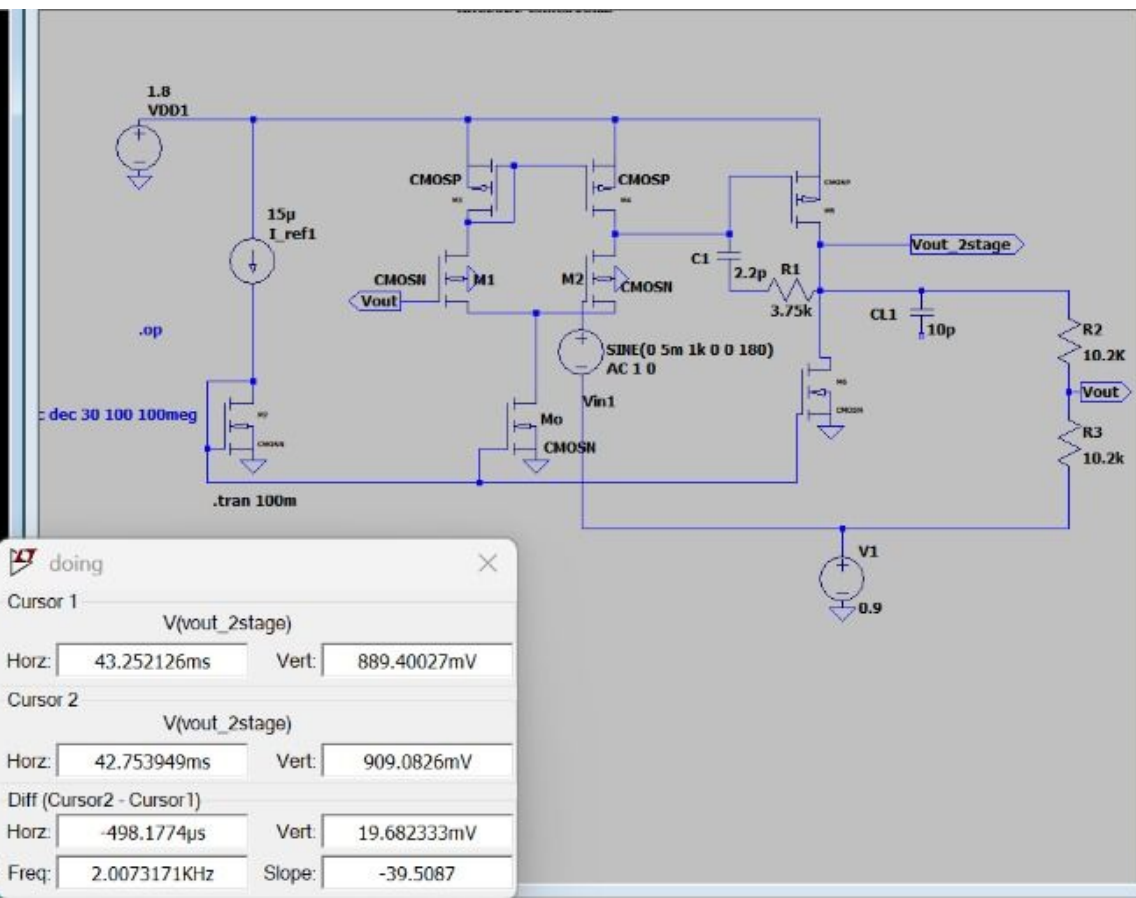

Name :	m3	m4	m5
Model :	cmosp	cmosp	cmosp
Id :	-1.95e-05	-1.95e-05	-1.59e-05
Vgs :	-6.22e-01	-6.22e-01	-6.46e-01
Vds :	-6.22e-01	-6.46e-01	-9.01e-01
Vbs :	-1.37e-01	-1.38e-01	-1.41e-01
Vth :	-3.81e-01	-3.81e-01	-3.79e-01
Vdsat :	-1.88e-01	-1.88e-01	-2.05e-01
Gm :	1.54e-04	1.55e-04	1.13e-04
Gds :	1.47e-06	1.44e-06	9.46e-07
Gmb	4.19e-05	4.19e-05	3.06e-05
Cbd :	0.00e+00	0.00e+00	0.00e+00
Cbs :	0.00e+00	0.00e+00	0.00e+00
Cgsov :	6.43e-15	6.43e-15	4.29e-15
Cgdov :	6.43e-15	6.43e-15	4.29e-15
Cgbov :	8.41e-19	8.41e-19	8.41e-19
dQgdVgb :	7.28e-14	7.28e-14	4.85e-14
dQgdVdb :	-6.34e-15	-6.34e-15	-4.21e-15
dQgdVsb :	-6.60e-14	-6.60e-14	-4.41e-14
dQddVgb :	-3.03e-14	-3.03e-14	-2.02e-14
dQddVdb :	6.39e-15	6.39e-15	4.25e-15
dQddVsb :	3.06e-14	3.06e-14	2.04e-14
dQbdVgb :	-1.21e-14	-1.21e-14	-8.08e-15
dQbdVdb :	-1.52e-17	-1.17e-17	2.95e-18
dQbdVsb :	-1.70e-15	-1.69e-15	-1.03e-15

Total elapsed time: 0.135 seconds.

Semiconductor Device Operating Points:

--- BSIM3 MOSFETS ---

Name:	m1	m2	mo	m7	m6
Model:	cmosn	cmosn	cmosn	cmosn	cmosn
Id:	1.95e-05	1.95e-05	3.90e-05	1.50e-05	1.59e-05
Vgs:	6.57e-01	6.58e-01	5.85e-01	5.85e-01	5.85e-01
Vds:	9.36e-01	9.12e-01	2.42e-01	5.85e-01	8.99e-01
Vbs:	-2.42e-01	-2.42e-01	5.71e-02	9.06e-02	1.06e-01
Vth:	4.82e-01	4.82e-01	3.96e-01	3.84e-01	3.78e-01
Vdsat:	1.45e-01	1.45e-01	1.44e-01	1.50e-01	1.53e-01
Gm:	2.11e-04	2.11e-04	4.03e-04	1.49e-04	1.54e-04
Gds:	1.41e-06	1.42e-06	1.20e-05	1.24e-06	1.06e-06
Gmb	5.39e-05	5.40e-05	1.05e-04	3.69e-05	3.74e-05
Cbd:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cbs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cgsov:	3.62e-15	3.62e-15	7.24e-15	2.41e-15	2.41e-15
Cgdov:	3.62e-15	3.62e-15	7.24e-15	2.41e-15	2.41e-15
Cgbov:	8.66e-19	8.66e-19	8.66e-19	8.66e-19	8.66e-19
dQgdVgb:	3.36e-14	3.36e-14	6.85e-14	2.28e-14	2.28e-14
dQgdVdb:	-3.53e-15	-3.53e-15	-7.53e-15	-2.36e-15	-2.36e-15
dQgdVsb:	-2.85e-14	-2.85e-14	-5.85e-14	-1.97e-14	-1.97e-14
dQddVgb:	-1.43e-14	-1.43e-14	-2.90e-14	-9.53e-15	-9.53e-15
dQddVdb:	3.57e-15	3.58e-15	7.60e-15	2.39e-15	2.38e-15
dQddVsb:	1.37e-14	1.37e-14	2.78e-14	9.19e-15	9.15e-15
dQbdVgb:	-5.12e-15	-5.11e-15	-1.06e-14	-3.70e-15	-3.72e-15
dQbdVdb:	7.45e-18	7.26e-18	-4.33e-16	2.43e-19	6.43e-18
dQbdVsb:	-2.43e-15	-2.43e-15	-4.38e-15	-1.11e-15	-9.77e-16

Name :	m3	m4	m5
Model :	cmosp	cmosp	cmosp
Id :	-1.95e-05	-1.95e-05	-1.59e-05
Vgs :	-6.22e-01	-6.22e-01	-6.46e-01
Vds :	-6.22e-01	-6.46e-01	-9.01e-01
Vbs :	-1.37e-01	-1.38e-01	-1.41e-01
Vth :	-3.81e-01	-3.81e-01	-3.79e-01
Vdsat :	-1.88e-01	-1.88e-01	-2.05e-01
Gm :	1.54e-04	1.55e-04	1.13e-04
Gds :	1.47e-06	1.44e-06	9.46e-07
Gmb :	4.19e-05	4.19e-05	3.06e-05
Cbd :	0.00e+00	0.00e+00	0.00e+00
Cbs :	0.00e+00	0.00e+00	0.00e+00
Cgsov :	6.43e-15	6.43e-15	4.29e-15
Cgdov :	6.43e-15	6.43e-15	4.29e-15
Cgbov :	8.41e-19	8.41e-19	8.41e-19
dQgdVgb :	7.28e-14	7.28e-14	4.85e-14
dQgdVdb :	-6.34e-15	-6.34e-15	-4.21e-15
dQgdVsb :	-6.60e-14	-6.60e-14	-4.41e-14
dQddVgb :	-3.03e-14	-3.03e-14	-2.02e-14
dQddVdb :	6.39e-15	6.39e-15	4.25e-15
dQddVsb :	3.06e-14	3.06e-14	2.04e-14
dQbdVgb :	-1.21e-14	-1.21e-14	-8.08e-15
dQbdVdb :	-1.52e-17	-1.17e-17	2.95e-18
dQbdVsb :	-1.70e-15	-1.69e-15	-1.03e-15

Total elapsed time: 0.097 seconds.

Semiconductor Device Operating Points:

--- BSIM3 MOSFETS ---

Name:	m1	m2	m0	m7	m6
Model:	cmosn	cmosn	cmosn	cmosn	cmosn
Id:	1.95e-05	1.95e-05	3.90e-05	1.50e-05	1.59e-05
Vgs:	6.57e-01	6.58e-01	5.85e-01	5.85e-01	5.85e-01
Vds:	9.36e-01	9.12e-01	2.42e-01	5.85e-01	8.99e-01
Vbs:	-2.42e-01	-2.42e-01	5.71e-02	9.06e-02	1.06e-01
Vth:	4.82e-01	4.82e-01	3.96e-01	3.84e-01	3.78e-01
Vdsat:	1.45e-01	1.45e-01	1.44e-01	1.50e-01	1.53e-01
Gm:	2.11e-04	2.11e-04	4.03e-04	1.49e-04	1.54e-04
Gds:	1.41e-06	1.42e-06	1.20e-05	1.24e-06	1.06e-06
Gmb	5.39e-05	5.40e-05	1.05e-04	3.69e-05	3.74e-05
Cbd:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cbs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cgsov:	3.62e-15	3.62e-15	7.24e-15	2.41e-15	2.41e-15
Cgdov:	3.62e-15	3.62e-15	7.24e-15	2.41e-15	2.41e-15
Cgbov:	8.66e-19	8.66e-19	8.66e-19	8.66e-19	8.66e-19
dQgdVgb:	3.36e-14	3.36e-14	6.85e-14	2.28e-14	2.28e-14
dQgdVdb:	-3.53e-15	-3.53e-15	-7.53e-15	-2.36e-15	-2.36e-15
dQgdVsb:	-2.85e-14	-2.85e-14	-5.85e-14	-1.97e-14	-1.97e-14
dQddVgb:	-1.43e-14	-1.43e-14	-2.90e-14	-9.53e-15	-9.53e-15
dQddVdb:	3.57e-15	3.58e-15	7.60e-15	2.39e-15	2.38e-15
dQddVsb:	1.37e-14	1.37e-14	2.78e-14	9.19e-15	9.15e-15
dQbdVgb:	-5.12e-15	-5.11e-15	-1.06e-14	-3.70e-15	-3.72e-15
dQbdVdb:	7.45e-18	7.26e-18	-4.33e-16	2.43e-19	6.43e-18
dQbdVsb:	-2.43e-15	-2.43e-15	-4.38e-15	-1.11e-15	-9.77e-16